

# Delay On with 555

$$t(\text{secs}) = 1.1 \cdot R1 \cdot C1 / 1000$$

delay time ~ 11.5s

Where R is in K $\Omega$  and C is in  $\mu\text{F}$

